Building to a Computer

CS 2130: Computer Systems and Organization 1 September 17, 2025

Announcements

- Homework 2 due Monday
- Office hours most days!

Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we already know: &, |, ^, ~
- Operations we can build from gates: +, -
- Others we can build:

Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we already know: &, |, ^, ~
- Operations we can build from gates: +, -
- Others we can build:
- Ternary operator: ? :

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: z = x * y

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: z = x * y
- What about the following?
 - x = 1
 - x = 0

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: z = x * y
- What about the following?
 - x = 1
 - x = 0
- Single assignment: each variable can only be assigned a value once

Subtraction

$$z = x + \sim y + 1$$

$$a = ~y$$

 $b = a + 1$
 $z = x + b$

Each of our comparisons in code are straightforward to build:

== - xor then nor bits of output

Each of our comparisons in code are straightforward to build:

- == xor then nor bits of output
- != same as == without not of output

Each of our comparisons in code are straightforward to build:

- == xor then nor bits of output
- != same as == without not of output
- < consider x < 0

Each of our comparisons in code are straightforward to build:

- == xor then nor bits of output
- != same as == without not of output
- \bullet < consider x < 0
- >, <=, => are similar

Indexing

Indexing with square brackets: []

- Register bank (or register file) an array of registers
 - Can programmatically pick one based on index
 - I.e., can determine which register while running
- Two important operations:
 x = R[i] Read from a register
 R[j] = y Write to a register

Reading

x = R[i] - connect output of registers to x based on index i



Aside: 4-input Mux

How do we build a 4-input mux? How many wires should i be?

Writing

R[j] = y - connect y to input of registers based on index j



Aside: Creating ==0 gates

How do we build gates that check for j == w?

Need one more thing to build computers

Memory and Storage

Registers

≈ KiB

- 6 gates each, \approx 24 transistors
- Efficient, fast
- Expensive!
- Ex: local variables

These do not persist between power cycles

Memory and Storage

Memory

 $\approx \text{GiB}$

- Two main types: SRAM, DRAM
- DRAM: 1 transistor, 1 capacitor per bit
- DRAM is cheaper, simpler to build
- Ex: data structures, local variables

These do not persist between power cycles

Memory and Storage

m Disk m pprox GiB-TiB

- Two main types: flash (solid state), magnetic disk
- Magnetic drive
 - Platter with physical arm above and below
 - Cheap to build
 - Very slow! Physically move arm while disk spins
- Ex: files

Data on disk does persist between power cycles

Putting it all together

Our story so far

- Information modeled by voltage through wires (1 vs 0)
- Transistors
- Gates: & / ~
- Multi-bit values: representing integers, floating point numbers
- Multi-bit operations using circuits
- Storing results using registers, clocks
- Memory

Code

How do we run code? What do we need?

Consider the following code:

```
8: x = 16
9: y = x
10: x += y
```

. . .

What is the value of x after line 10?

Bookkeeping


What do we need to keep track of?

- Code the program we are running
 - RAM (Random Access Memory)
- State things that may change value (i.e., variables)
 - Register file can read and write values each cycle
- Program Counter (PC) where we are in our code
 - Single register byte number in memory for next instruction

Building a Computer






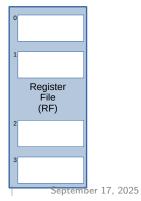


Encoding Instructions

Encoding of Instructions (icode or opcode)

Numeric mapping from icode to operation

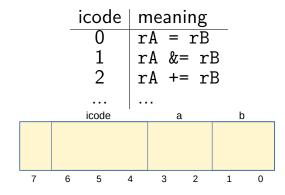

Building a Computer

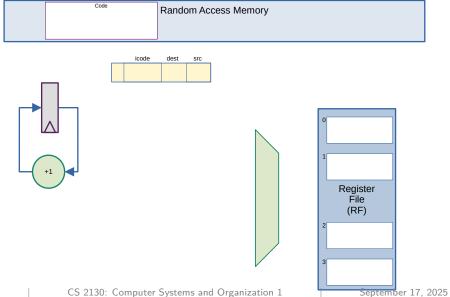







Building a Computer





